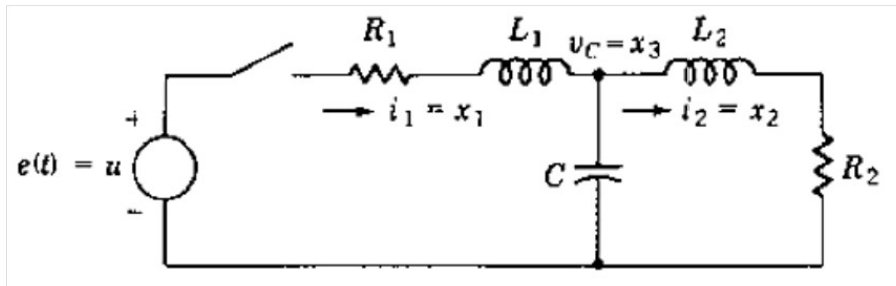


Lab Session 04

Exercise:

Question 1:

Obtain the state space representation for the system shown below. Solve the resulting state equations using MATLAB *ode45* function (write complete script). Plot the inductor current i_1 and i_2 and the capacitor voltage v_c as marked in the figure with respect to time for $t = 0$ to 500 sec considering the following values of R , L and C and write in your words about what you observed by looking at plots. [Hint: Refer lecture 3 for the possible observations about this question.]
[Use separate A4 sheets for plots and attach it with this document]



System Parameters:

$$R_1 = R_2 = 10$$

$$L_1 = L_2 = 1$$

$$C = 5$$

$$e = 50$$

Write your answers below this line
