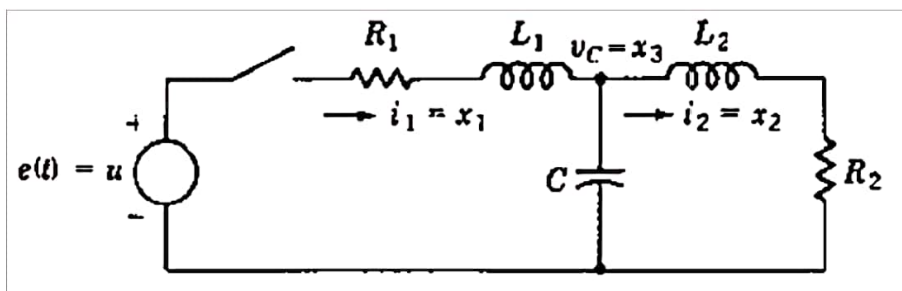


**Lab Session 04****Exercise:****Question 1:**

Obtain the state space representation for the system shown below. Solve the resulting state equations using MATLAB *ode45* function (write complete script). Plot the inductor current  $i_1$  and  $i_2$  and the capacitor voltage  $v_c$  as marked in the figure with respect to time for  $t = 0$  to 500 sec considering the following values of  $R$ ,  $L$  and  $C$  and write in your words about what you observed by looking at plots.

[Hint: Refer lecture 3 for the possible observations about this question.]

[Use separate A4 sheets for plots and attach it with this document]

**System Parameters:**

$$R_1 = R_2 = 10$$

$$L_1 = L_2 = 1$$

$$C = 5$$

$$e = 50$$

Write your answers below this line

For Mesh 1:-

$$R_1 i_1 + L_1 \frac{di_1}{dt} + \frac{1}{C} (i_1 - i_2) = e \quad \text{--- (A)}$$

For Mesh 2:-

$$\frac{1}{C} (i_1 - i_2) = L_2 \frac{di_2}{dt} + R_2 i_2 \quad \text{--- (B)}$$

State Variables:-

$$x_1 = i_1, \quad x_2 = i_2, \quad x_3 = v_c$$

Now,

$$\dot{x}_1 = \frac{e}{L_1} - \frac{R_1}{L_1} x_1 - \frac{1}{L_1} x_3 \quad \text{--- (1)}$$

$$\dot{x}_2 = \frac{1}{L_2} x_3 - \frac{R_2}{L_2} x_2 \quad \text{--- (2)}$$

$$\dot{x}_3 = \frac{1}{C} x_1 - \frac{1}{C} x_2 \quad \text{--- (3)}$$

FUNCTION SCRIPT:-RLC.m :-

function dxdt = RLC(t,x)

R1 = 10 ; R2 = 10;

L1 = 1 ; L2 = 1;

C = 5 ; e = 50;

dxdt(1,1) = e/L1 - R1\*x(1)/L1 - x(3)/L1;




dxdt(2,1) = x(3)/L2 - R2\*x(2)/L2;

dxdt(3,1) = x(1)/C - x(2)/C;

end

PROGRAM SCRIPT:-

```
1- clear, close, clc
2- [t,x] = ode45('RLC', [0 500], [0; 0; 0; 0]);
3- figure
4- subplot(3,1,1);
5- plot(t, x(:,1), 'Line Width', 1.5);
6- ylabel('Current (i1)'); xlabel('Time (t)');
7- title('Current at Inductor (L1)');
8- legend('i1'); grid;
9- subplot(3,1,2);
10- plot(t, x(:,2), 'k', 'Line Width', 1.5);
11- ylabel('Current (i2)'); xlabel('Time (t)');
12- title('Current at Inductor (L2)');
13- legend('i2'); grid;
14- subplot(3,1,3);
15- plot(t, x(:,3), 'r', 'Line Width', 1.5);
16- ylabel('Voltage (Vc)'); xlabel('Time (t)');
17- title('Voltage at Capacitor (C)');
18- legend('Vc'); grid;
```

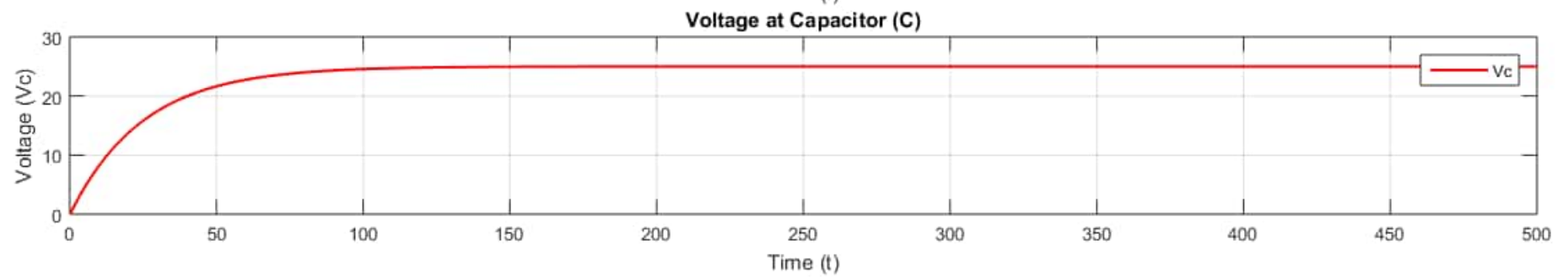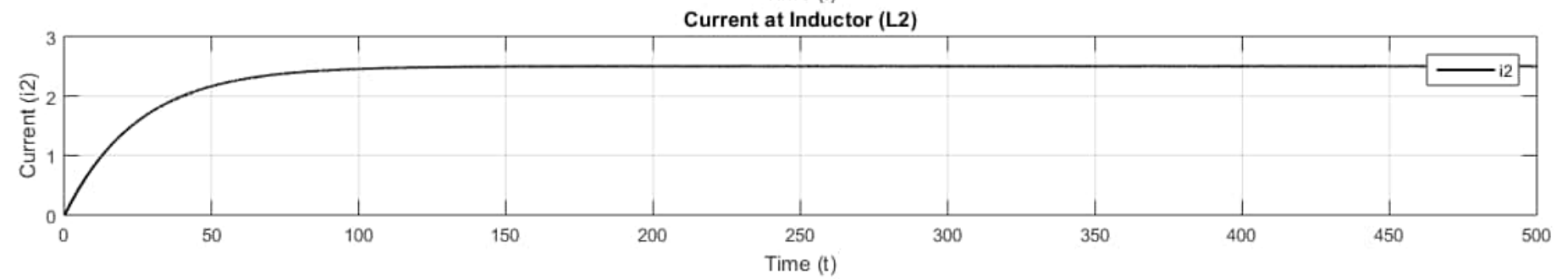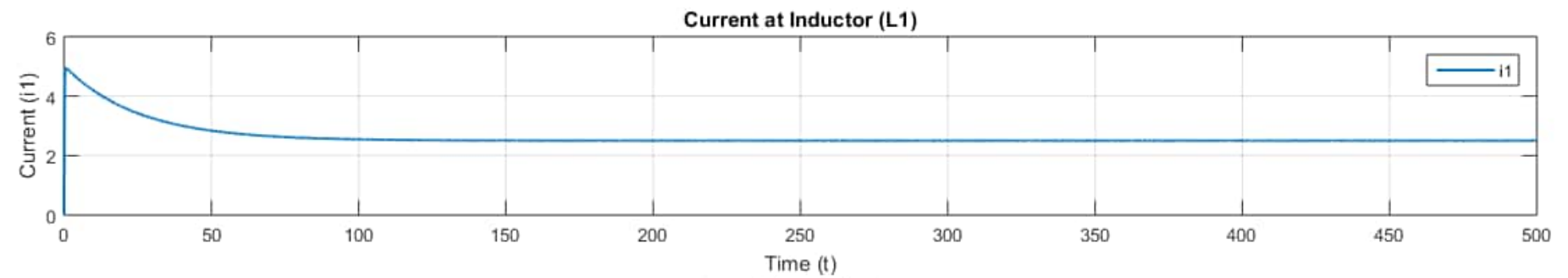

## OBSERVATIONS :-

### At Inductor $L_1$ :-

Current ( $i_1$ ) at inductor ( $L_1$ ) starts with a constant value and decays exponentially, it achieves stability ~~linear~~ after some time and remains constant.

### At Inductor $L_2$ :-

Current ( $i_2$ ) at inductor ( $L_2$ ) starts with zero and increases exponentially, it achieves stability after some time and remains constant.

### At Capacitor $C$ :-

Voltage ( $V_c$ ) at capacitor ( $C$ ) starts with zero and increases exponentially, it achieves stability after some time and remains constant