

## **Lab Session 05**

### **Exercise:**

#### **Question 1:**


Using MATLAB SIMULINK, model a system present in lab session 3 and 4. Use the same values of R, L, C and M, B, K as given in these lab sessions. Attach the created SIMULINK model with this document. Plot the same outputs as mentioned in lab session 4 and 5.



*[Use separate A4 sheets for plots and attach it with this document]*

*Nothing to write below this line. Just attach model and plots with this document.*

---

# MKB Simulink Model

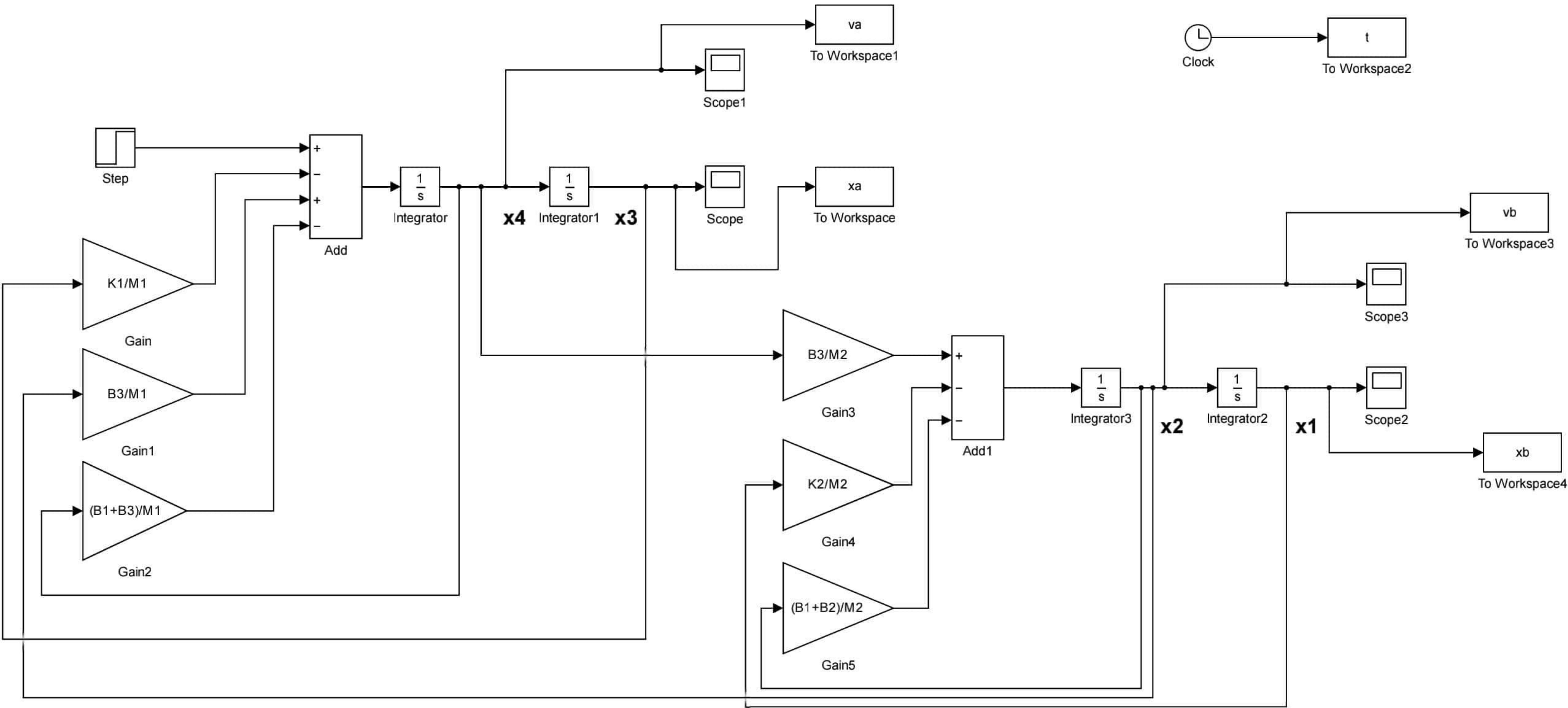

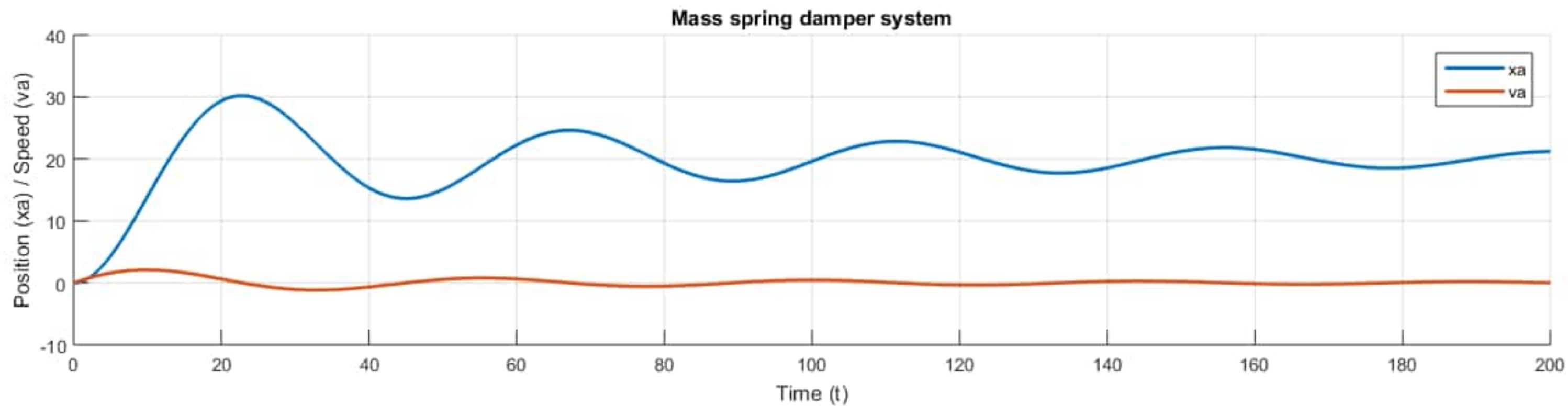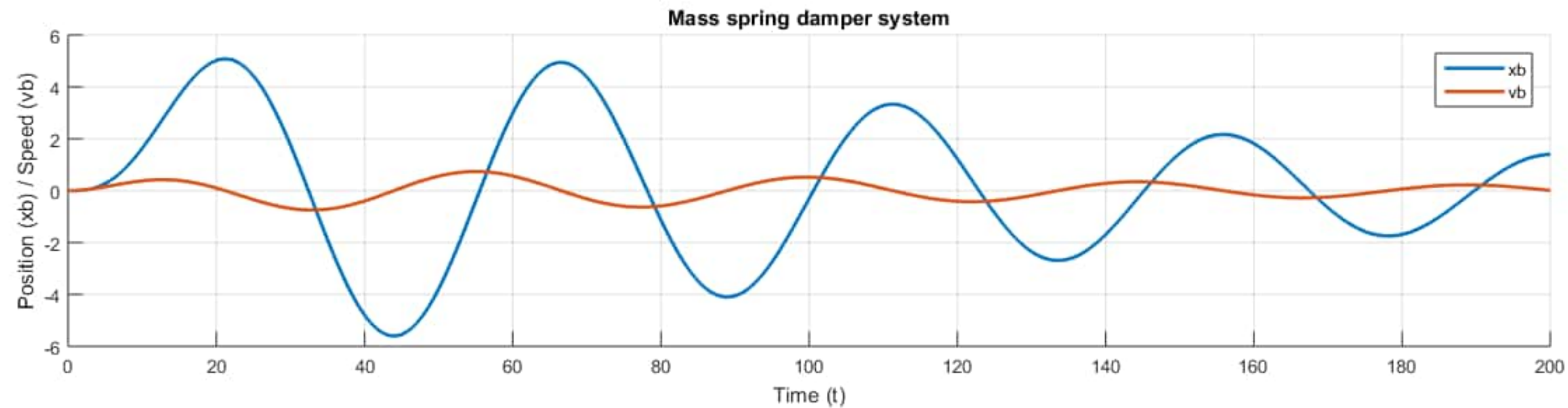

# RLC Simulink Model

